



- [Blog](#)
- [MAKE Magazine](#)
- [Videos/Podcasts](#)
- [Make: Projects](#)
- [Forum/Community](#)
- [Maker Shed Store](#)

LOG IN JOIN US

[Get Started »](#)

[Contribute »](#)

[Search](#)

[« Back to category](#)

Page 1 of 1

# Bacteria Battery



From MAKE Magazine

This project first appeared on the pages of MAKE magazine.

*Microbial fuel cells generate electricity from "metal-breathing" bacteria in ordinary mud.*

Author: [Ashley Franks](#) Time required: **1 to 2 hours** Difficulty: **Easy**

★ 1    💬 x 4    ✅ x 4

[Tweet](#)

[Send](#)

Microorganisms often get a bad name because some of them cause disease. But many have useful abilities, from making beer, cheese, and wine to processing waste and cleaning up toxic chemicals. One type of bacteria, discovered in 1987 by Derek Lovley, can generate electricity. Here's how you can find bacteria like these in a local pond and put them to work.

Most non-photosynthesizing bacteria, like all animals, get their energy from the cellular respiration process, which converts glucose and oxygen to water and carbon dioxide. Oxygen works as an oxidizer, which means it accepts electrons as it combines with other chemicals in

[View](#)

[Edit](#)

[History](#)

Image metadata



## Biology

Biology Science.

8 Step-by-step Guides

[Start a New Guide](#)

reactions. But special bacteria underground have no oxygen to breathe. Instead, they produce energy for their growth by transferring electrons to clumps of rust and other surrounding metal oxides, in a process called dissimilatory metal reduction. We now know that these electric bacteria are found in mud virtually everywhere on Earth, as well as in soil and compost heaps.

A microbial fuel cell (MFC) does the same thing as a battery: drive electrons from an anode to a cathode through chemical oxidation/reduction reactions. What makes MFCs different is that they run on organic substrate and bacteria.

“Metal-breathing” (Geobacter) bacteria at the anode carry out the oxidation reaction, converting plant and animal debris in the mud into electricity and carbon dioxide. Electrons flow through wires to a cathode sitting in water above the mud, where they combine with oxygen to complete the circuit. The bacteria are highly efficient in this arrangement and can produce electricity continuously for many months or even years.

[Read More](#)

## Sections

[Make your own MFC.](#)  
[Microbe Power](#)

## Tools

- Drill , hand-held, electric, with 1/8" bit *(optional) if drilling your own lids*
-  Multimeter *(optional) for testing power*
- Pair of Rubber Gloves
- Shovel or Trowel
-  Wire strippers *(optional) if not using pre-stripped wires from the kit*

## Relevant Parts

-  MudWatt MFC Kit *Item #MKKT01 from Maker Shed, \$45. Includes all materials below, except mud. You can also build MFCs from scratch, minus the Hacker Board.*
- Container , waterproof, with tight lid
-  Grommet (2) , rubber sized to seal marine wire through holes drilled in container lid

## Relevant Parts (continued)

-  MuddWatt Hacker Board *includes voltage-boosting chip, 8-pin socket, 22µF capacitor, resistors, and red LED that blinks when bacteria generate power. (NOTE: some of the photos show the MuddWatt Explorer board instead.)*
- Mud *Almost any mud with organic compounds will work. Try freshwater ponds or streams, brackish swamps and inlets, or saltwater marshes. Try to find mud that bubbles when disturbed or smells like rotten eggs — both are good indicators of anaerobic bacteria (but don't worry, your MFC won't smell). You can also use soil (just dig down a foot) or compost from the warm middle of a heap.*
- Marine Wire (2 lengths) , 16-20 gauge, 4" longer than container height *Using 2 different colors helps.*

[View large](#)  
[Image metadata](#)



## Step 1 — Make your own MFC. [Edit](#)


Mix your mud (or soil or compost) to saturation with water and put a ½" layer into the bottom of your container. You can experiment by adding extra ingredients; see <http://keegotech.com/community/education> for ideas.

Cut the 2 pieces of graphite fiber cloth to fit the container. Be careful not to disperse the fibers in the air because they can cause short circuits in household electrical equipment.

Strip 4" from one end of each piece of marine wire, and weave each through a piece of graphite cloth. Strip the other ends ½" and thread each through a grommet. Drill the lid of the container to fit the grommets.

[View large](#)  
[Image metadata](#)



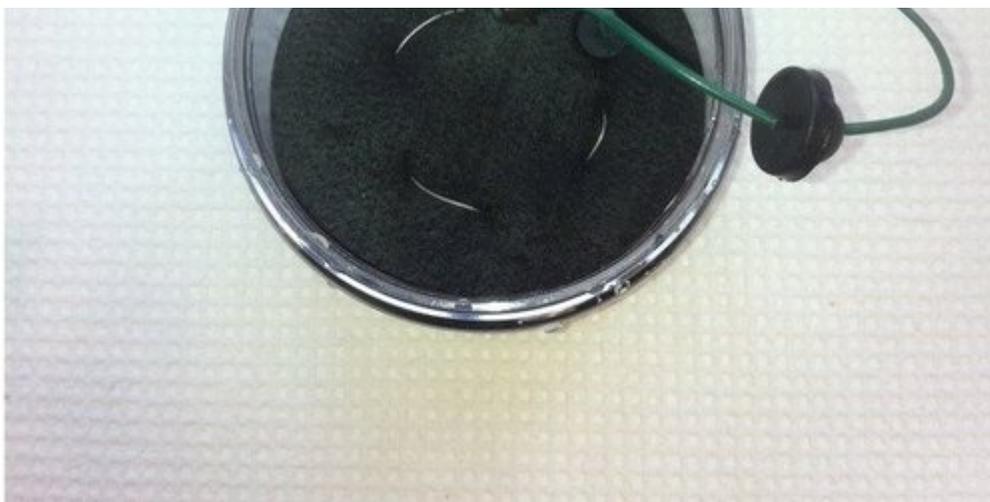

## Step 2

Edit 

Lay one graphite cloth on top of the mud with its wire sticking up; this will be the anode. Cover it with  $\frac{1}{2}$ " more mud and let it settle for a few minutes.

[View large image metadata](#)



## Step 3

Edit 

For the cathode, place the other graphite cloth on top of the mud, with its wire also pointing up. Avoid covering the cathode cloth with any mud, and gently pour a little water on top to moisten it.

If the cathode doesn't sink in water (it may have air bubbles in it), try putting a few small rocks on it to keep it from floating.

Close the container, sealing the grommets into the holes in the lid such that the wires stick out. It may



[View large](#)  
[Image metadata](#)



help to gently twist the wires counterclockwise one turn before screwing on the top.




## Step 4

[Edit](#)

Attach the 2 wires to the MudWatt Hacker Board's 8-pin socket: anode to the (-) pin and cathode to the (+) pin.


Attach the Hacker Board to the lid of your container using the provided adhesive pad.

[View large](#)  
[Image metadata](#)

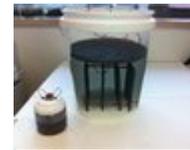

## Step 5 – Microbe Power

[Edit](#)

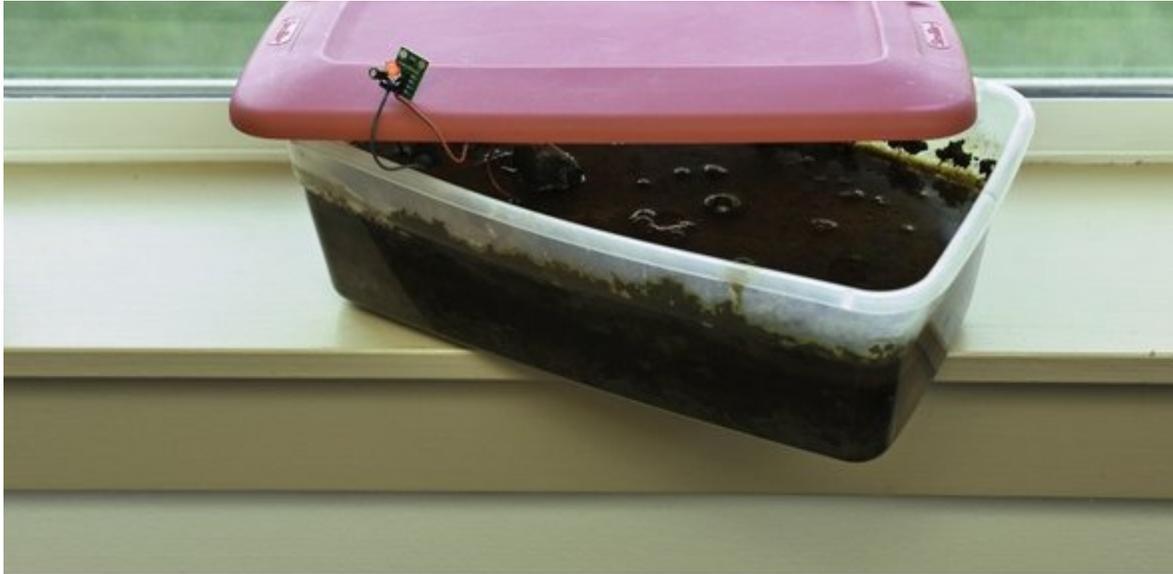

Within 3–10 days, the MFC will generally produce enough power to make the LED blink; the more power, the faster the blinking. Keep your MFC warm and moist inside to help the bacteria grow and produce the most power.

Try adding a very small amount of table salt to the water to increase conductivity if the voltages are too low.

The MudWatt Hacker Board boosts the bacteria's power to 2.4 volts, and its 8-pin socket lets you change a resistor value in the blinker circuit to optimize power to the LED. You can also power other devices that run on 3V or less. Download the instructions at [http://keegotech.com/community/Hacker\\_Bo...](http://keegotech.com/community/Hacker_Bo...) and see <http://keegotech.com/forum> for more ideas.

Power generated by an MFC is a product of its electrode surface area, so once you have your first one running, don't be afraid to go large.

By simply configuring 2 electrodes correctly in mud, soil, or compost, anyone anywhere can harness naturally occurring bacteria to provide continuous, non-polluting, carbon-neutral electricity.

---

This project first appeared in **MAKE Volume 30**, page 140.

For more information, check out the [Biology category page](#).

**I did it! Success!**

[Post to Facebook](#)   [Share on Twitter](#)

## Comments

---

### Guide

Where did you get the graphite cloth? Is it the same as carbon fibre matting?

Rick Baker, May 25

The graphite cloth can be found on KeegoTech's website if you want to buy it separately, or as part of the MudWatt kit (which you can buy from the Maker Shed.) The cathode and anode are basically pieces of graphite cloth with the marine wire already woven in. I found other sources on the Internet when I was making this for the magazine, but mostly people selling it on eBay or in really huge quantities-- no reliable retailer for small quantities. But if you're willing to look on the Internet you might find another supplier.

Max, May 25

Carbon fibre matting is similar to cloth. Any type of carbon cloth, carbon fiber or solid graphite can be used as an electrode. Avoid any material with wet proofing as this will prevent the bacteria making an electrical connection with the electrode.

Ashley Franks , May 26

---

How stable is this energy source? How long can it produce energy for? Also, what is the maximum amount of energy it can produce? Thanks!

Barbara Shi, Jun 23

---